

Adam Frazee  
Homework 6  
10/22/2105  
CSE 278

**B.11** [5] [4.2, B.2, B.3] Assume that X consists of 3 bits,  $x_2 x_1 x_0$ . Write four logic functions that are true if and only if

- X contains only one 0

$$F = \bar{x}_2 \cdot x_1 \cdot x_0 + x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0$$

$x_2$	$x_1$	$x_0$	result
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- X contains an even number of 0s

$$F = \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot \bar{x}_1 \cdot x_0 + \bar{x}_2 \cdot x_1 \cdot x_0 + x_2 \cdot x_1 \cdot x_0$$

$x_2$	$x_1$	$x_0$	result
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- X when interpreted as an unsigned binary number is less than

$$F = \bar{x}_2$$

$x_2$	$x_1$	$x_0$	result
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

- X when interpreted as a signed (twos complement) number is negative

$$F = x_2$$

$x_2$	$x_1$	$x_0$	result
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

**B.14** [5] [B.2, B.3] Implement a switching network that has two data inputs (A and B), two data outputs (C and D), and a control input (S). If S equals 1, the network is in pass-through mode, and C should equal A, and D should equal B. If S equals 0, the network is in crossing mode, and C should equal B, and D should equal A.

